

Preliminaries: Combinational Logic



Chulyun Kim

* This material is based on the lecture slides provided by Morgan Kaufmann




Outline

- Truth Table
- Gates
- Decoder
- Multiplexor
- BUS
- ALU



Truth Table


INPUTS		OUTPUTS					
A	B	AND	NAND	OR	NOR	EXOR	EXNOR
0	0	0	1	0	1	0	1
0	1	0	1	1	0	1	0
1	0	0	1	1	0	1	0
1	1	1	0	1	0	0	1

 

Lamp - ON = "1"
Lamp - OFF = "0"

Switch A - Open = "0", Closed = "1"

Switch B - Open = "0", Closed = "1"

 

Lamp - ON = "1"
Lamp - OFF = "0"

Switch A - Open = "0", Closed = "1"

Switch B - Open = "0", Closed = "1"



Gates


• AND: $A \cdot B$ 


NAND: $\overline{A \cdot B}$ 

• OR: $A + B$ 

NOR: $\overline{A + B}$ 

• NOT: \overline{A} 

• XOR: $A \oplus B$ 

XNOR: $\overline{A \oplus B}$ 

• Example: $\overline{\overline{A} + B}$





How to Implement Output?

Input			Output		
A	B	C	P	Q	R
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	1	1	0



How Make One-Hot

Input			Output		
A	B	C	P	Q	R
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	0	1
1	1	1	0	0	0

$$P = \bar{A} \cdot B \cdot \bar{C}$$



How to Make One-Cold


Input			Output		
A	B	C	P	Q	R
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	1	1	1

$$P = A + \bar{B} + C$$

Disjunctive normal form (DNF)



 
- Combine one-hot clauses
 - Conjunction of literals \rightarrow one-hot clause
 - Disjunction of clauses \rightarrow combine one-hots



Conjunctive normal form (CNF)



 - Combine one-cold clauses
 - Disjunction of literals \rightarrow one-cold clause
 - Conjunction of clauses \rightarrow combine one-colds





Normal Form

- Conjunctive normal form (CNF)
 - it is a conjunction of one or more clauses, where a clause is a disjunction of literals

$$(A \vee B) \wedge (\neg B \vee C \vee \neg D) \wedge (D \vee \neg E)$$


- Disjunctive normal form (DNF)
 - it is a disjunction of one or more clauses, where a clause is a conjunction of literals

$$(A \wedge \neg B \wedge \neg C) \vee (\neg D \wedge E \wedge F)$$



Decoder

 - An n -bit input and 2^n outputs
- If the value of the input is i , then Out_i will be true and all other outputs will be false




a. A 3-bit decoder

Inputs			Outputs							
12	11	10	Out7	Out6	Out5	Out4	Out3	Out2	Out1	Out0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

b. The truth table for a 3-bit decoder



2-bit Decoder

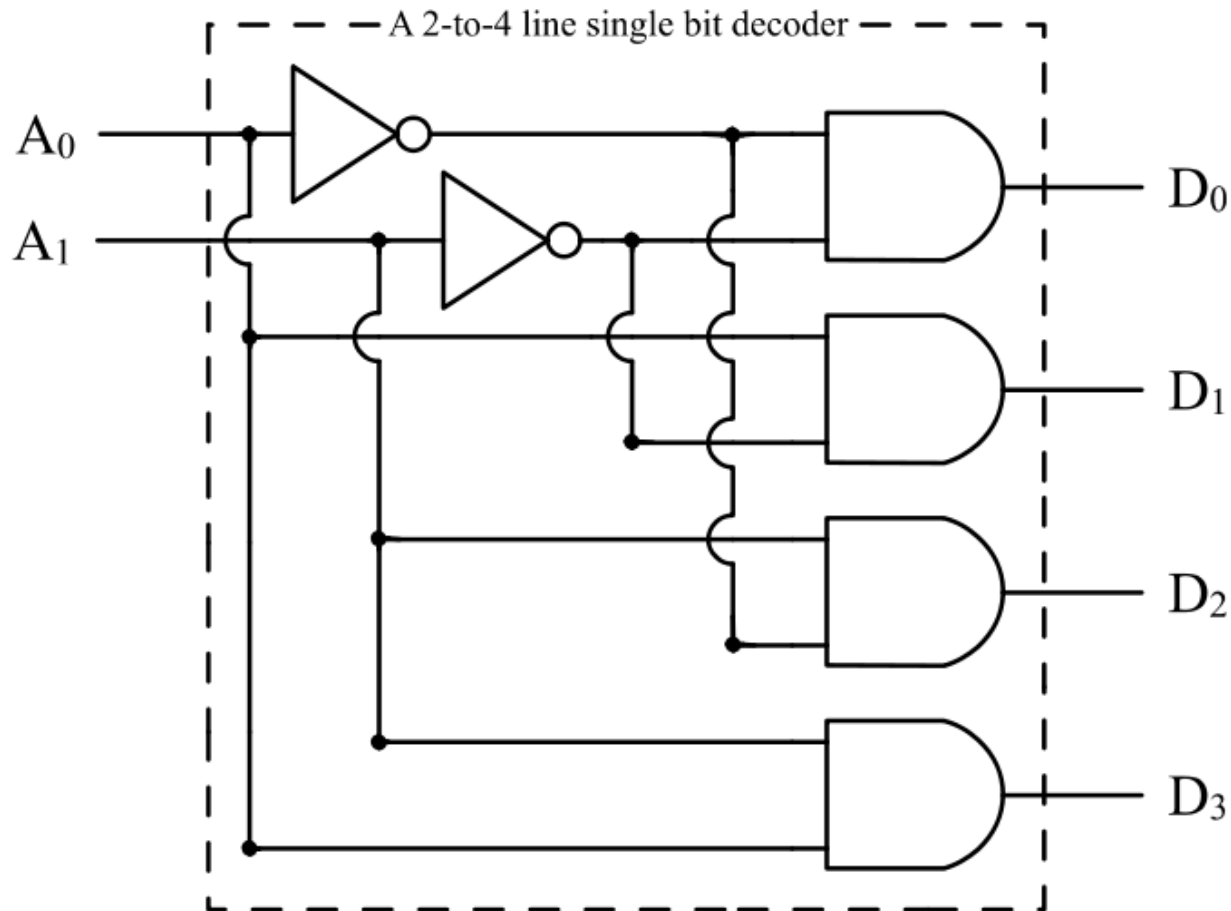

Truth Table

A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Minterm Equations

$$D_0 = \overline{A_1} \cdot \overline{A_0}$$

$$D_1 = \overline{A_1} \cdot A_0$$

$$D_2 = A_1 \cdot \overline{A_0}$$

$$D_3 = A_1 \cdot A_0$$





Example

- 3-bit Decoder




Multiplexor

  - Selector
 - Its output is one of the inputs that is selected by a control
 - If there are n data inputs, there will need to be $\lceil \log_2 n \rceil$ selector inputs
- 2-input Multiplexor (or 1-bit Multiplexor)
 - $C = (A \cdot \overline{S}) + (B \cdot S)$





n-input Multiplexor

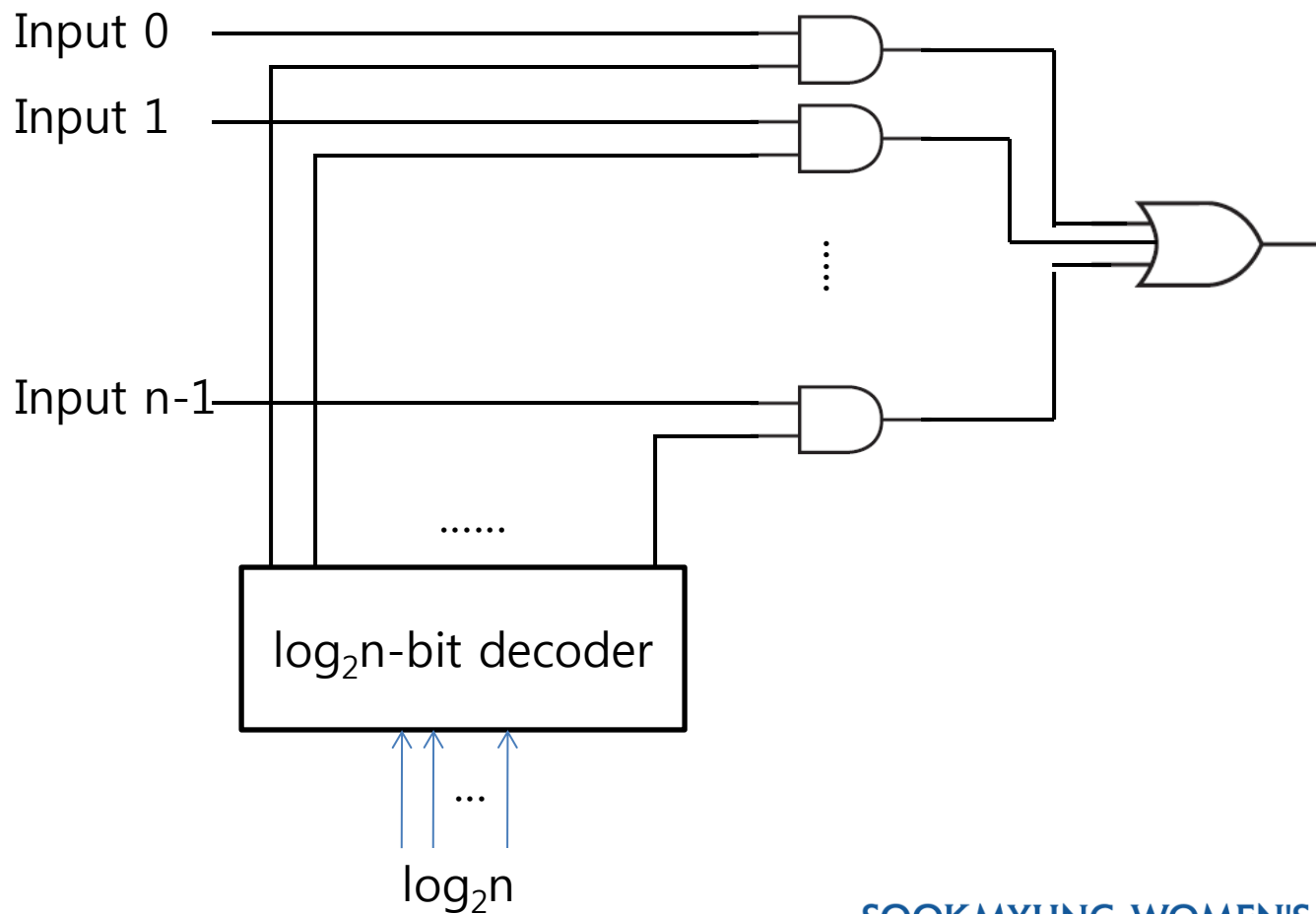






Example

- 4-input (or 2-bit) Multiplexor



BUS

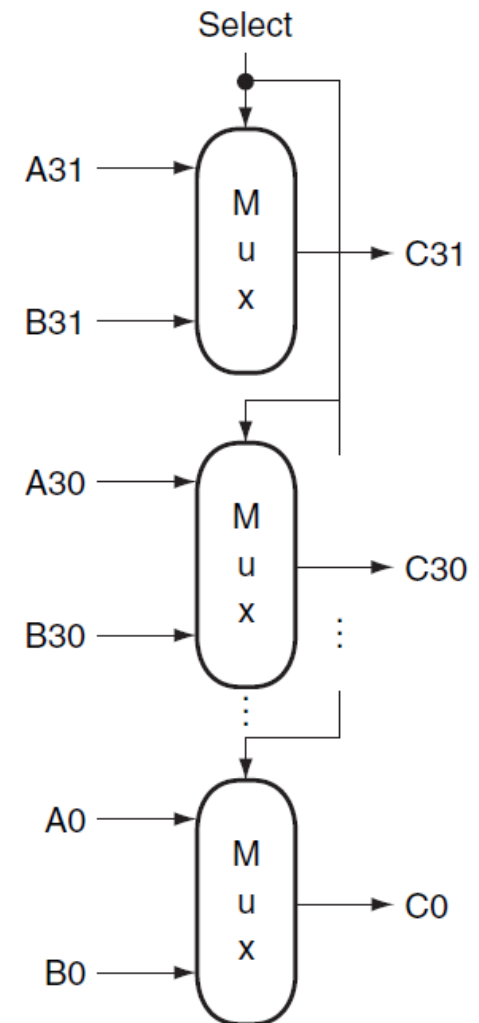  - A collection of data lines that is treated together as a single logical signal
- The term bus is also used to indicate a shared collection of lines with multiple sources






ALU: Arithmetic Logic Unit

- Device that performs
 - Arithmetic operations like addition and subtraction
 - Logical operations like AND and OR



Logical Unit for AND/OR

- 1-bit Logical Unit for AND/OR

 

- Example
 - 2-bit Logical Unit for AND/OR




1-bit Adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$



1-bit Adder


- Sum = $(a \cdot \overline{b} \cdot \overline{\text{CarryIn}}) + (\overline{a} \cdot b \cdot \overline{\text{CarryIn}}) + (\overline{a} \cdot \overline{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$
 $= (a \cdot \overline{b} + \overline{a} \cdot b) \cdot \overline{\text{CarryIn}} + (\overline{a} \cdot \overline{b} + a \cdot b) \cdot \text{CarryIn}$
 $= a \oplus b \cdot \overline{\text{CarryIn}} + a \oplus b \cdot \text{CarryIn}$
 $= (a \oplus b) \oplus \text{CarryIn}$

 




1-bit Adder

- $$\begin{aligned}\text{CarryOut} &= (\overline{a} \cdot b \cdot \text{CarryIn}) + (a \cdot \overline{b} \cdot \text{CarryIn}) \\ &\quad + (a \cdot b \cdot \overline{\text{CarryIn}}) + (a \cdot b \cdot \text{CarryIn}) \\ &= (\overline{a} \cdot b + a \cdot \overline{b}) \cdot \text{CarryIn} + a \cdot b \cdot (\overline{\text{CarryIn}} + \text{CarryIn}) \\ &= (a \oplus b) \cdot \text{CarryIn} + a \cdot b\end{aligned}$$

 


1-bit ALU

 




32-bit ALU

- Array of 1-bit ALUs

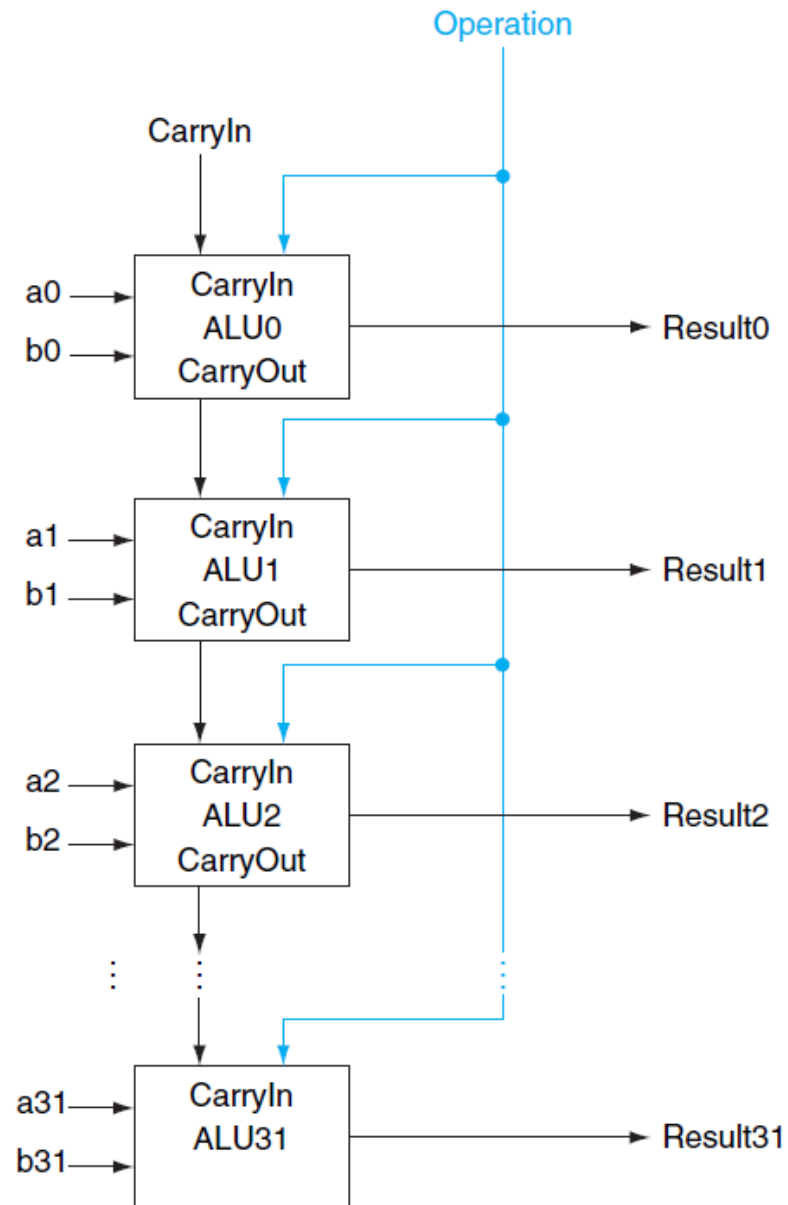

1-bit ALU AND/OR/ADD/NOT

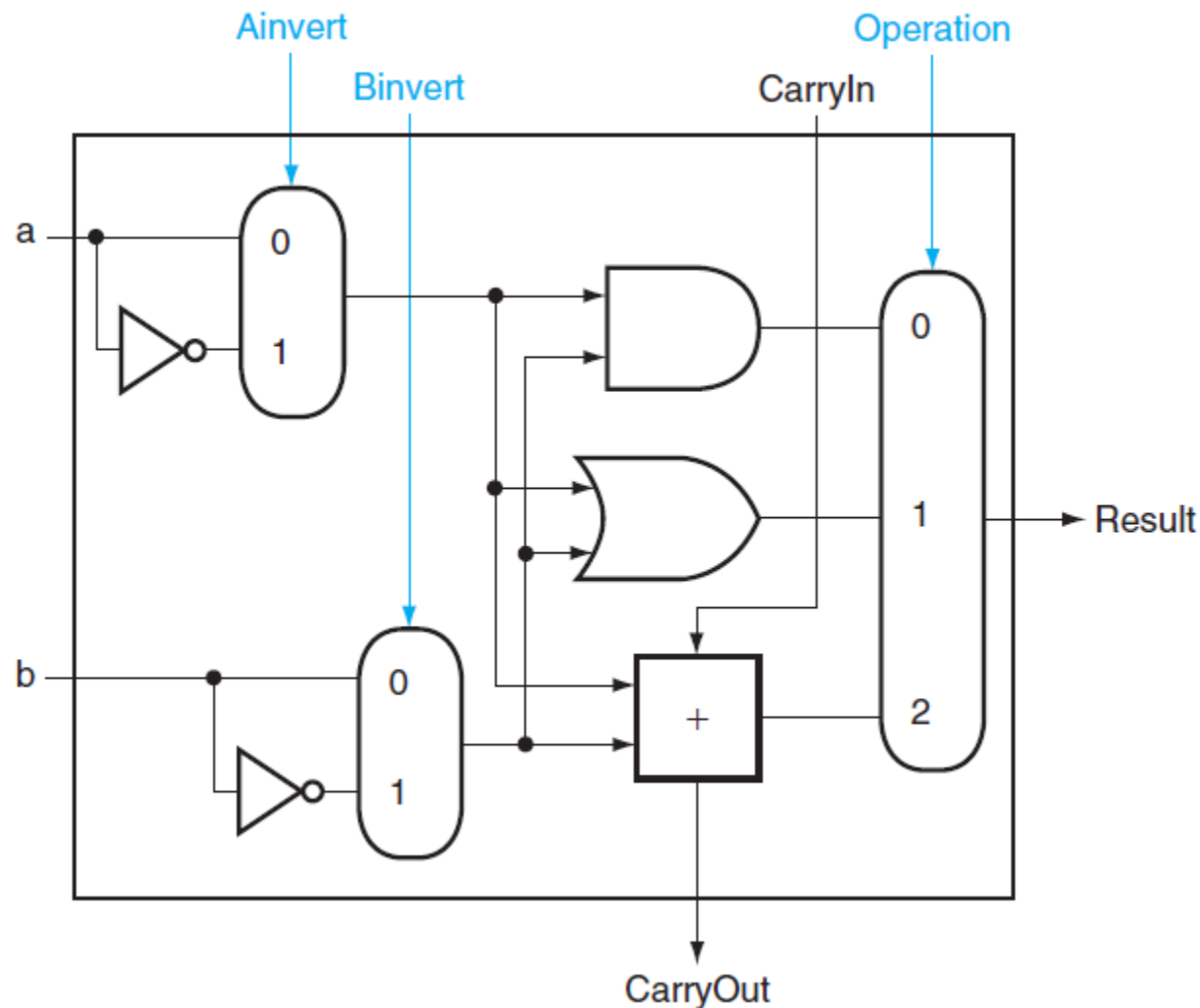




Example


- 2-bit ALU

1-bit ALU AND/OR/ADD/NOT/SLT

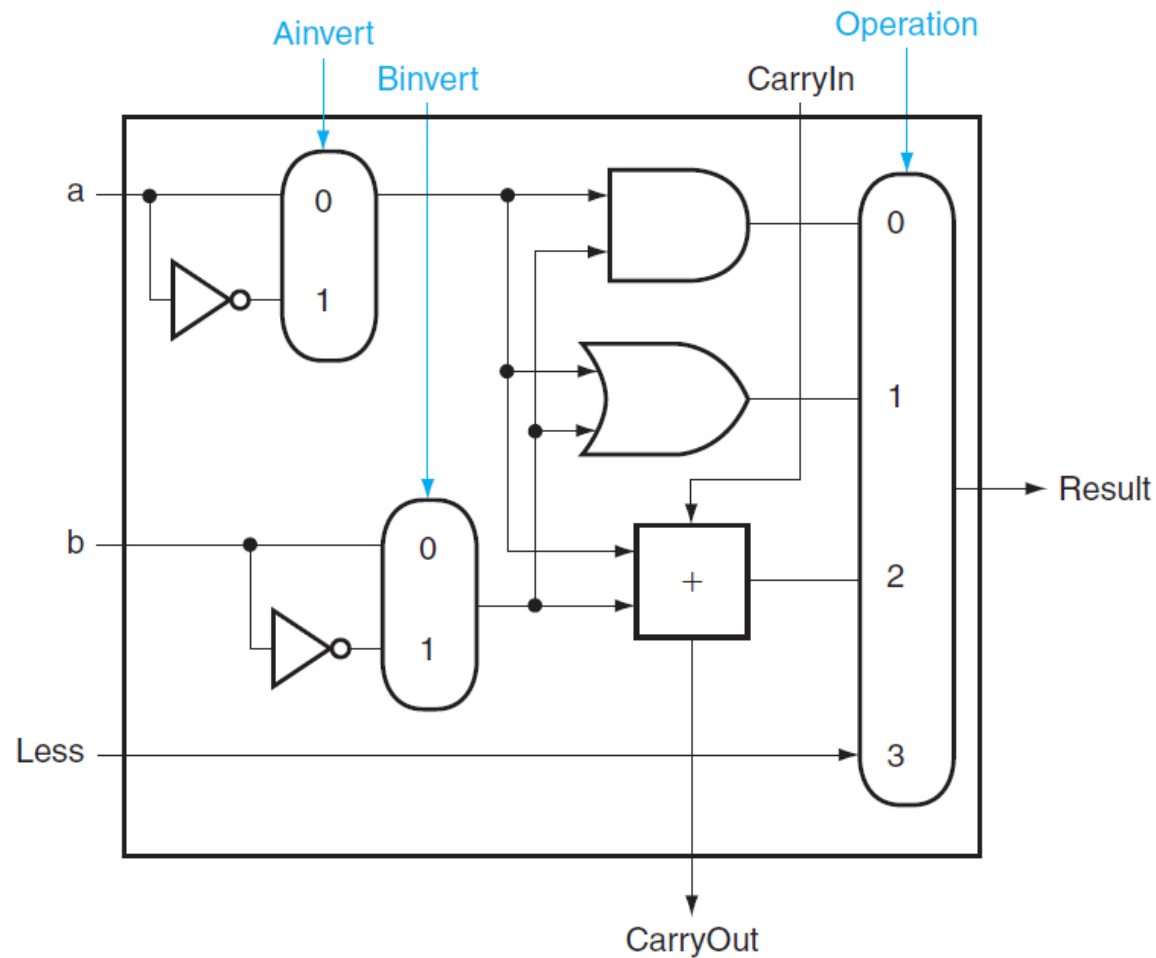




Final 32-bit ALU

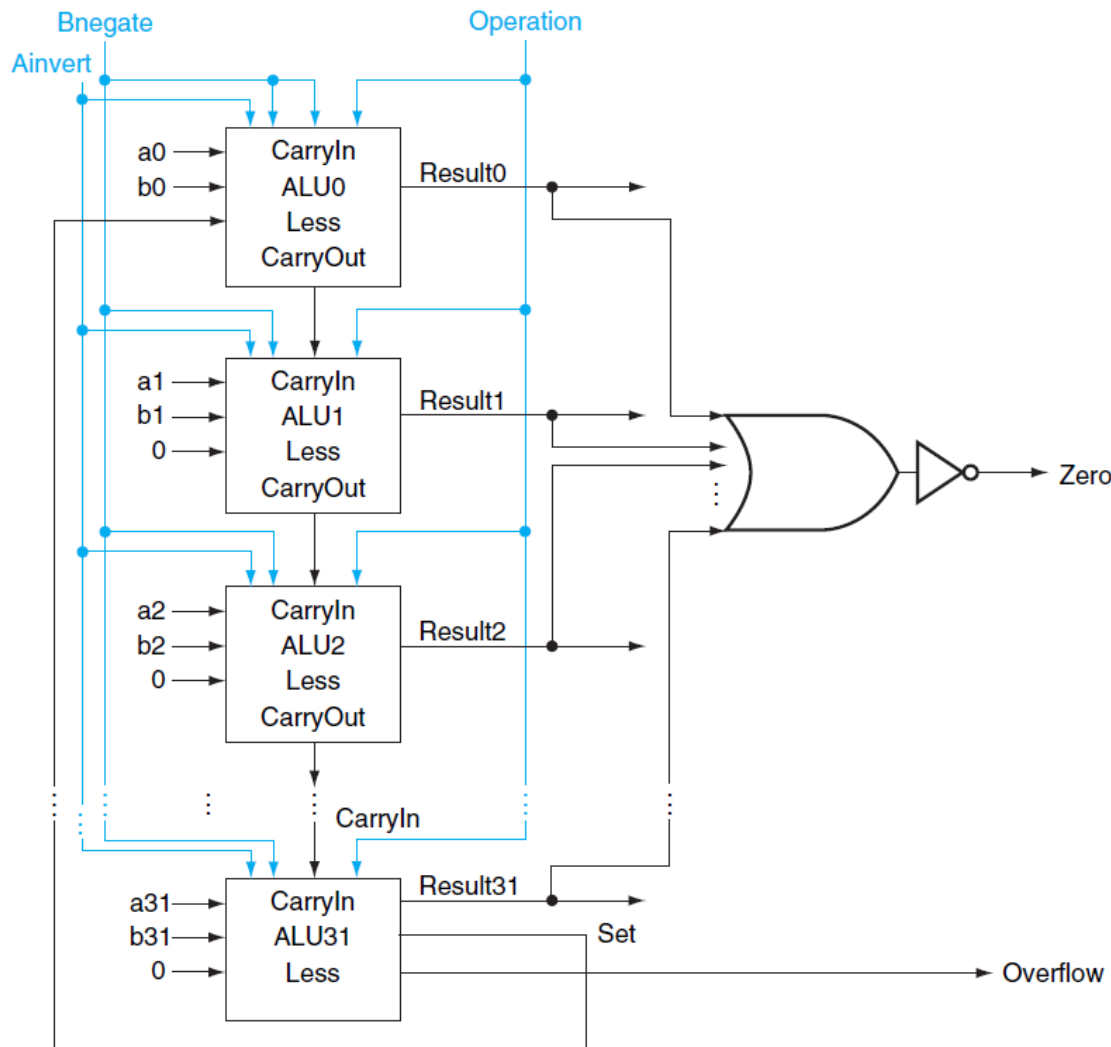


ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

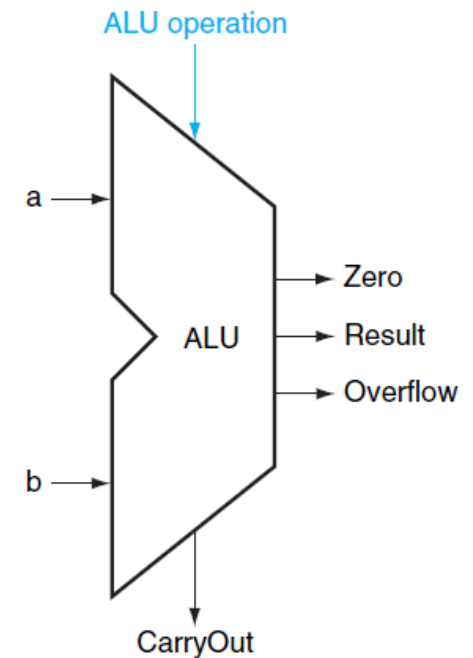



Clocks

 
- Clocks are needed to decide when a state should be updated
 - Free-running signal with a fixed cycle time
- Edge-triggered clocking
 - All state changes occur on a clock edge





S-R Latch


 
- Set-Reset Latch
 - Unclocked
 - If $S=1$ (or asserted) and $R=0$ (or deasserted)
 - $Q=1$ and $\bar{Q}=0$
 - If $S=0$ and $R=1$
 - $Q=0$ and $\bar{Q}=1$
 - If $S=0$ and $R=0$
 - The last values will continue





D Latch

  
- A clock input
- The change of state is triggered by the clock
- If clock is deasserted (or 0)
 - The last values will continue
- If clock is asserted (or 1)
 - Q will be D
 - \bar{Q} will be \bar{D}



D flip-flop with a falling edge trigger



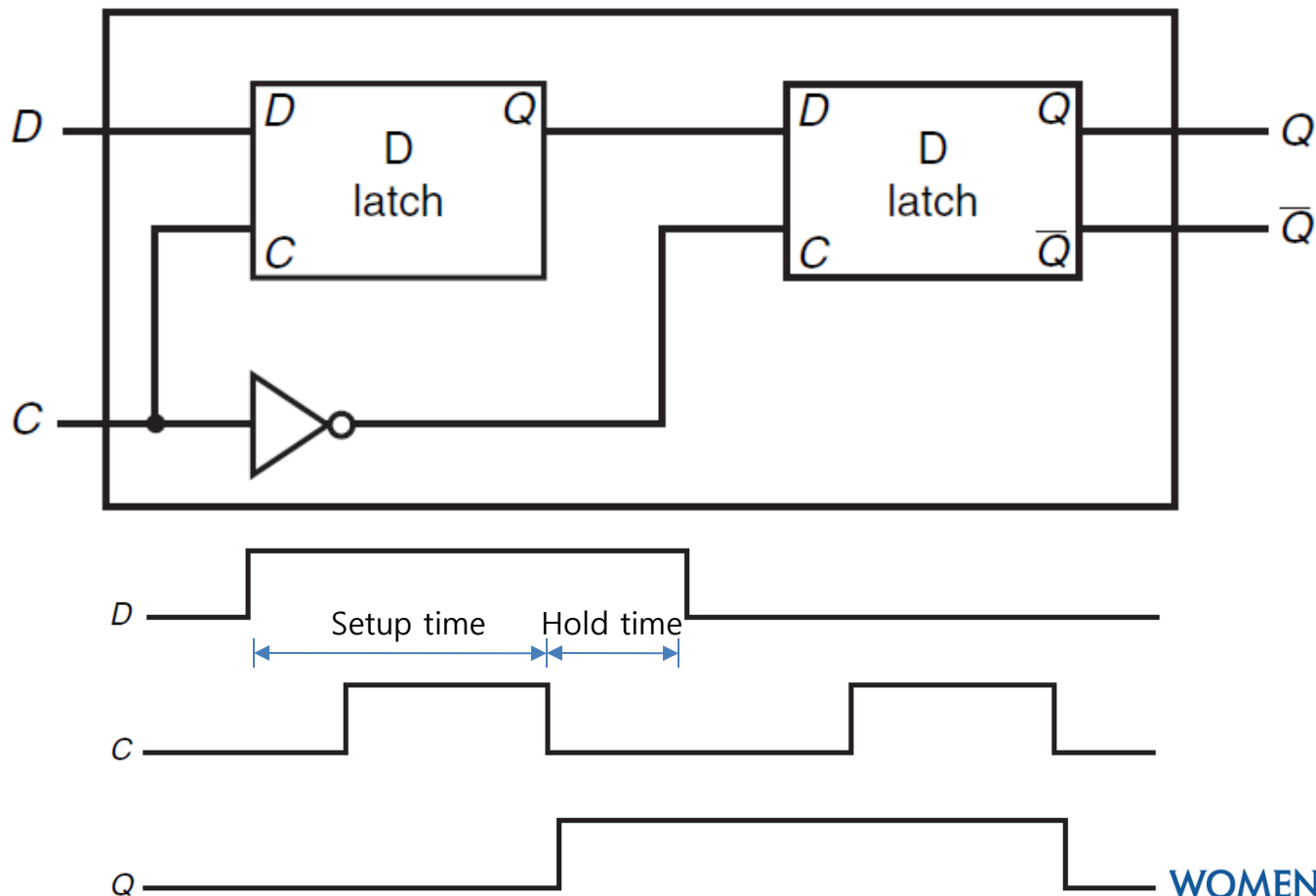
- Outputs change *only on the clock edge*






Register Files

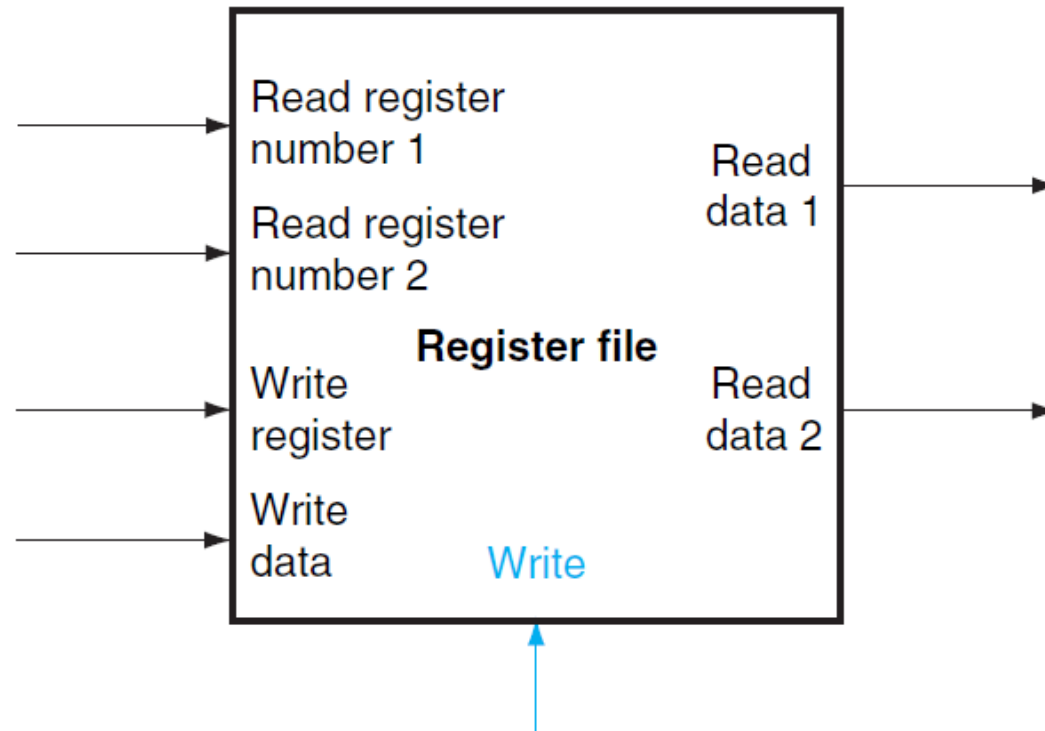- A set of registers that can be read and written



Read

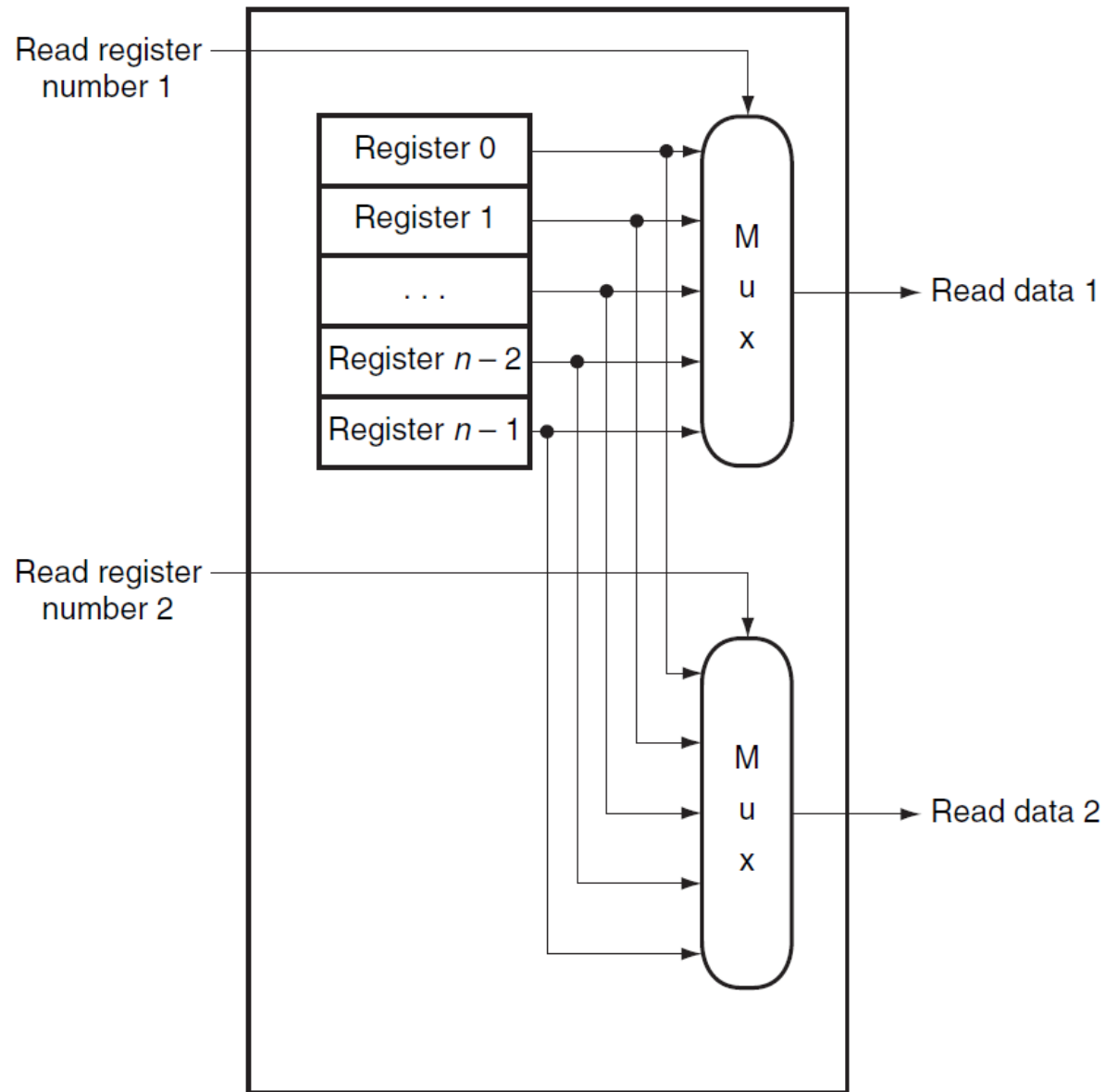

Write

